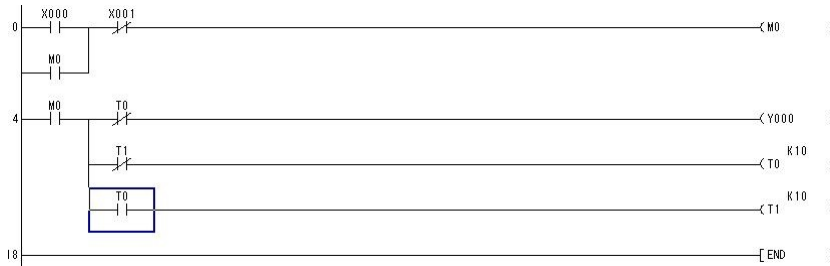


100408 電気保全技術


○技能検定によく出る回路

・フリッカ回路 (ONOFF/ OFFON) [PG001] [PG002]

> ONOFF




> OFFON

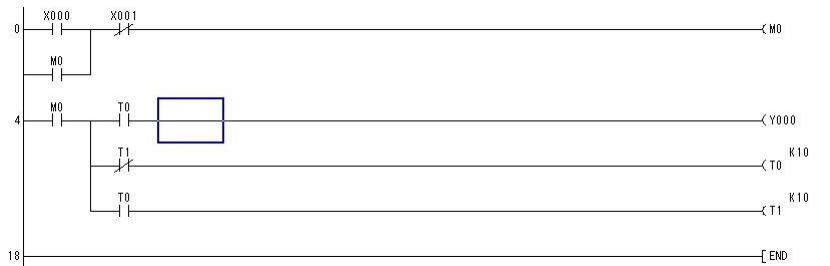


・ PLS/PLF 命令 [PG003] [PG004]


> PLS

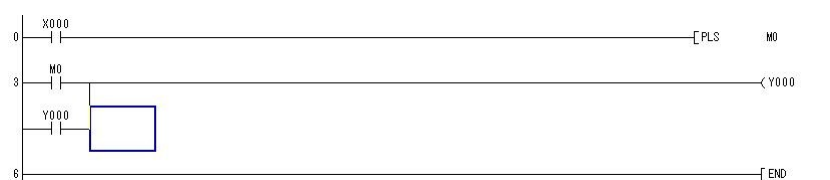

> PLF

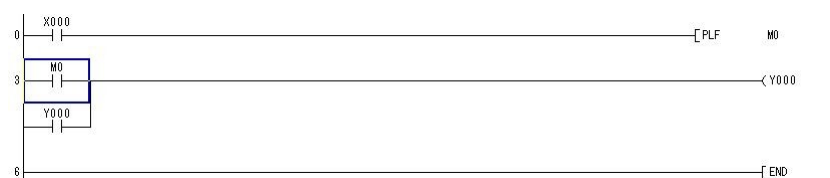


・ ALT 命令 [PG005]

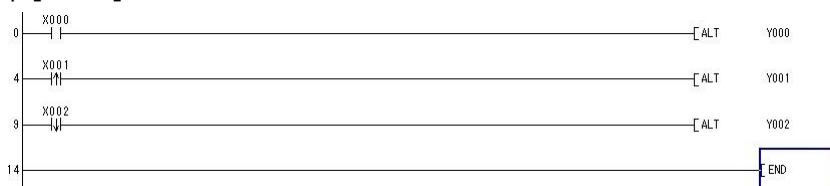


・ INC (P) /DEC (P) 命令 [PG006]

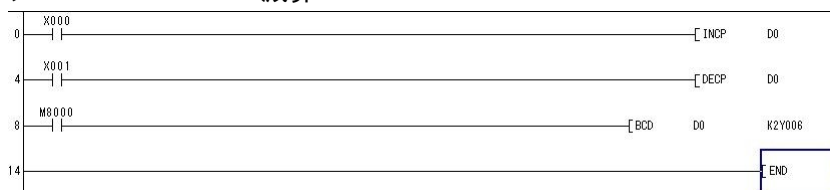- > INC → 加算命令
- > INCP → 1 加算
- > DEC → 減算命令
- > DECP → 1 減算




100409 電気保全技術
○技能検定過去問題


・平成17年度2級仕様1

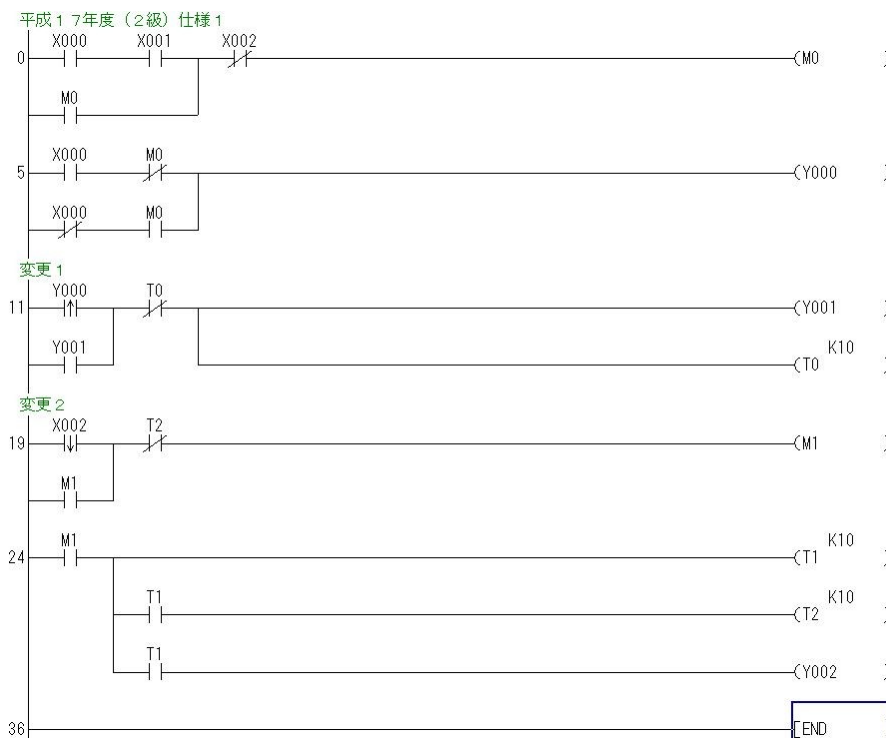


・平成17年度2級仕様2

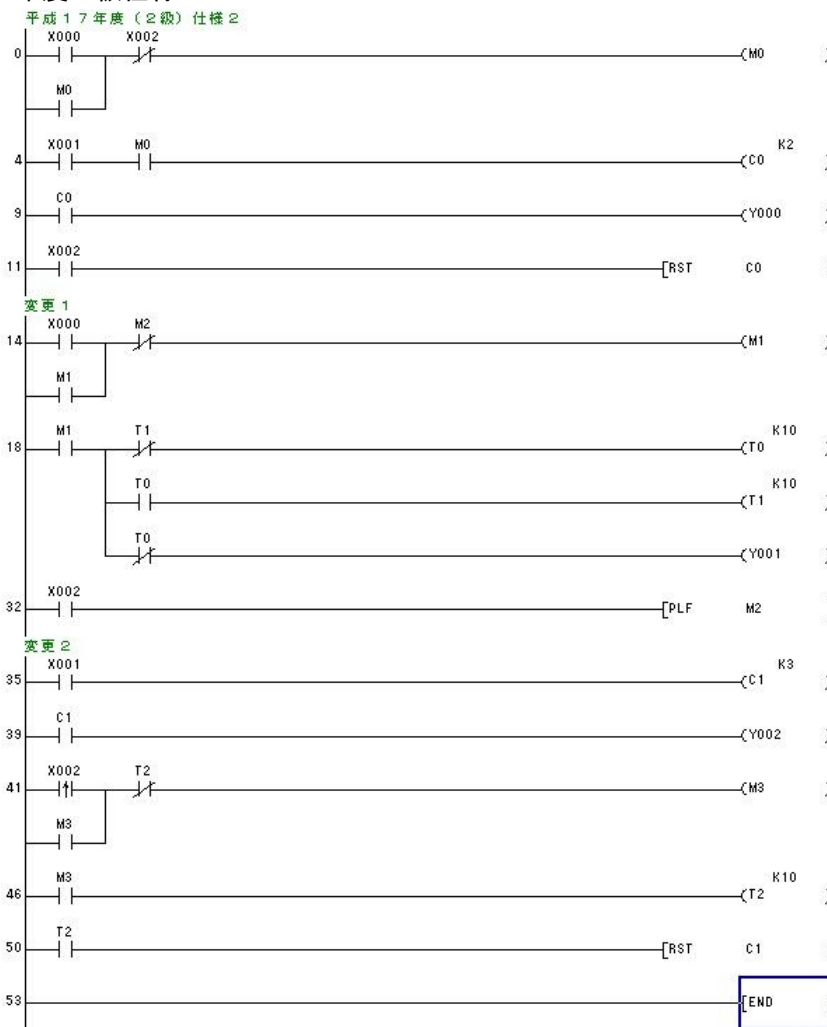


・平成18年度2級仕様1

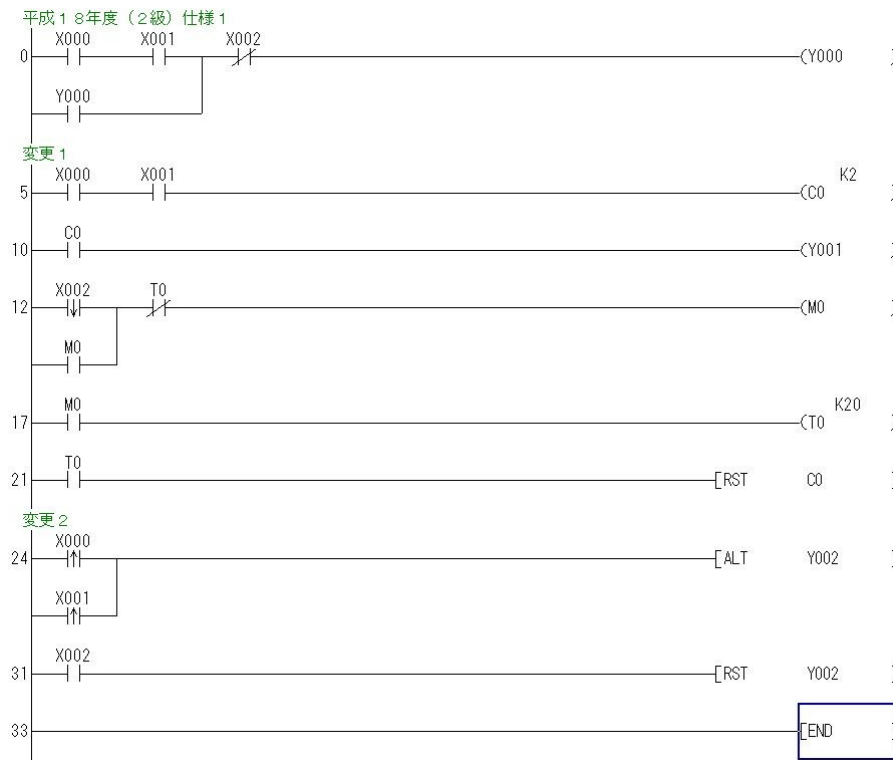


・平成18年度2級仕様2

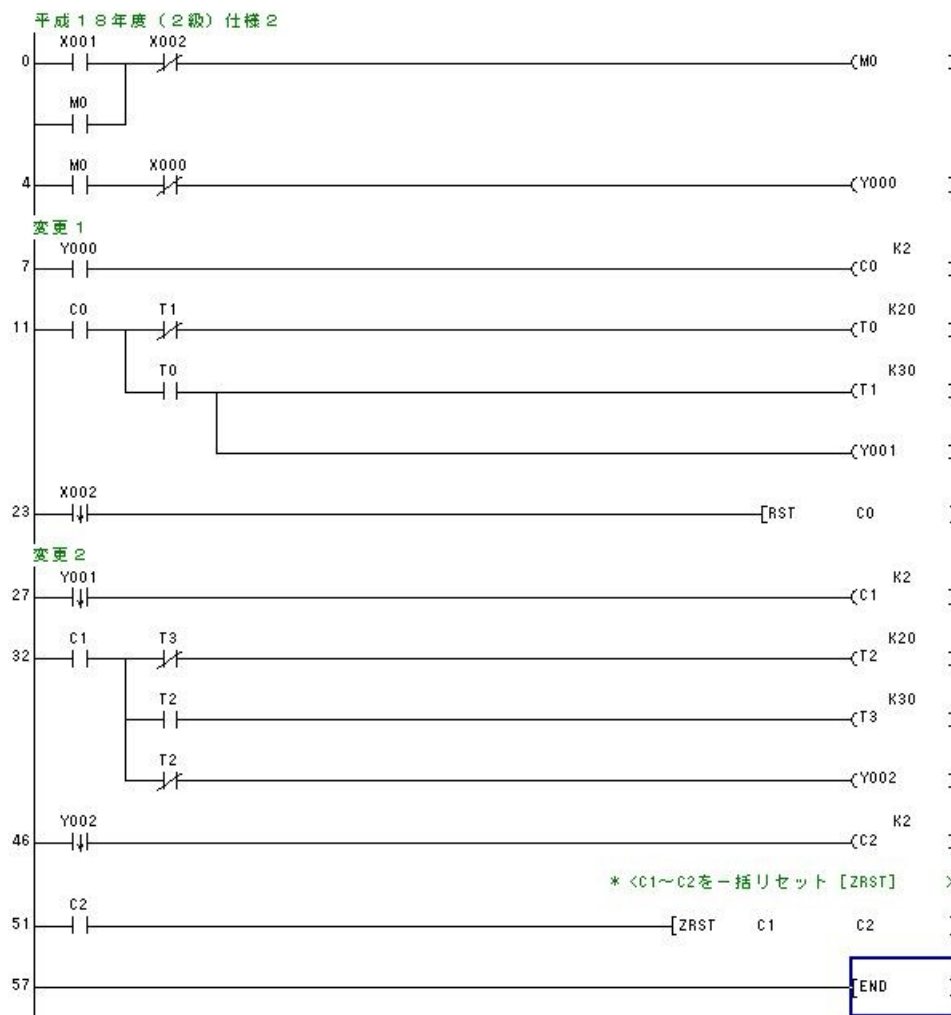


・平成19年度2級仕様1

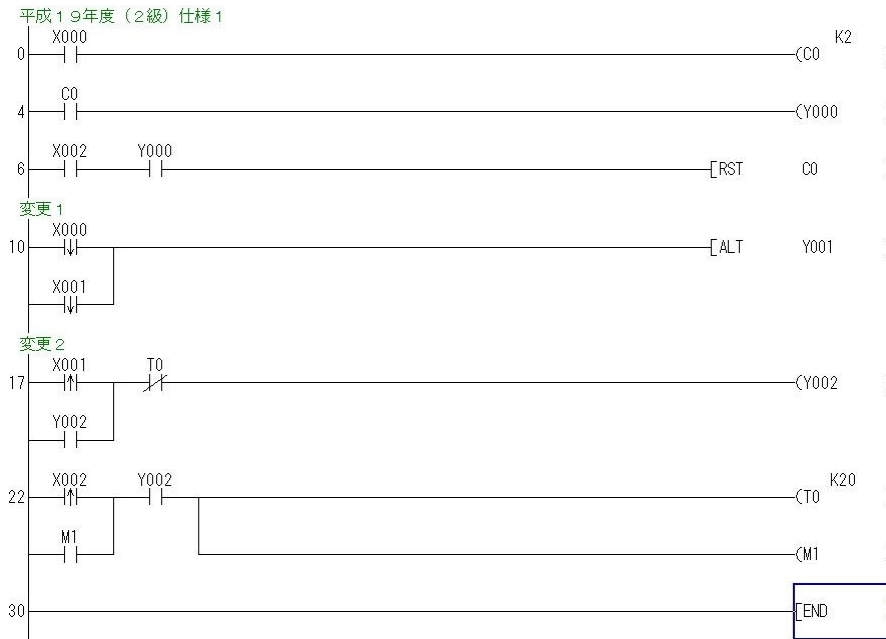

・平成19年度2級仕様2

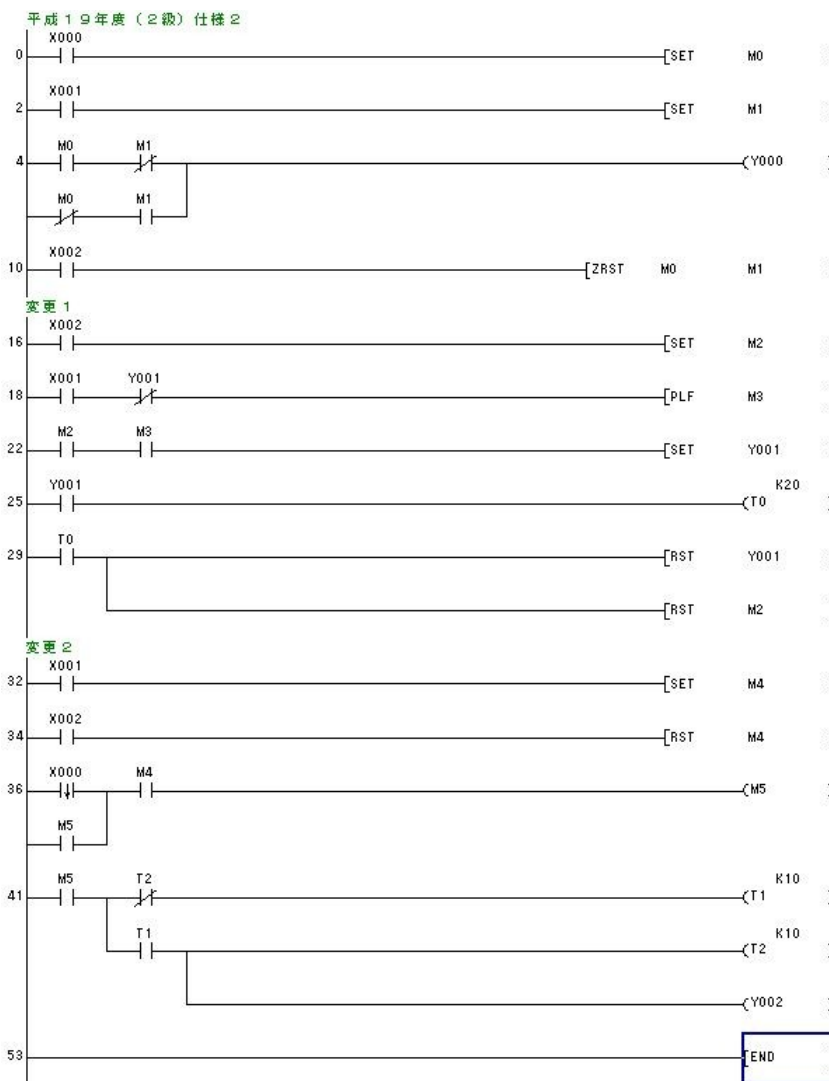

・平成20年度2級仕様1

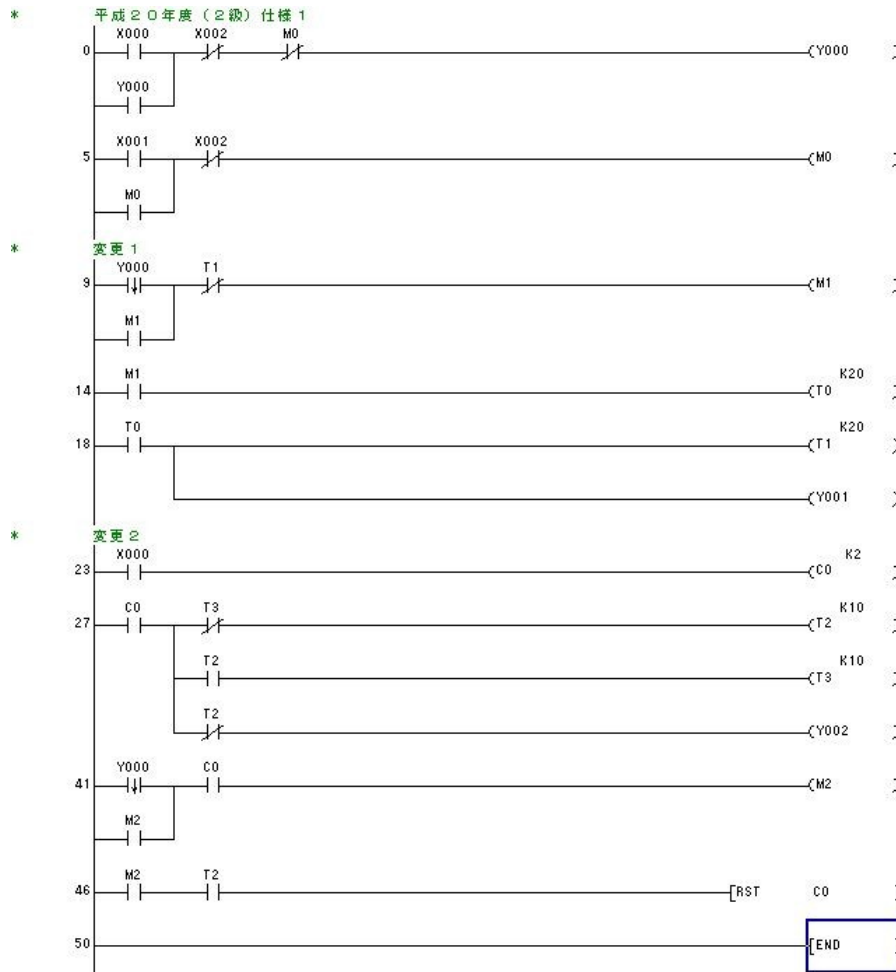

・平成20年度2級仕様2

